

O Level Combined Physics MCQs

Current and DC Circuits Test 2.0

Q1

A wire of resistance R has length L and cross-sectional area A . The wire is then stretched to twice its length and half its cross-sectional area. What is the resistance of the wire after it is being stretched?

A $\frac{1}{4}R$


B R

C $2R$

D $4R$

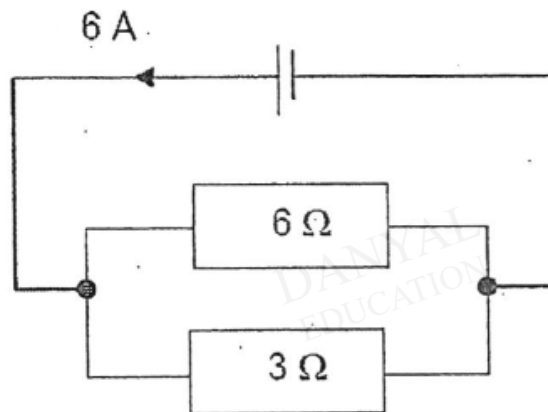Q2

What is the current flowing through the $3\ \Omega$ resistor as shown in the figure below?



A 1 A

B 2 A

C 3 A

D 4 A

Q3

What is the total charge that has passed through a bulb when an electric current of 5 A is flowing for 2 minutes?

A 2.5 C

B 10 C

C 24 C

D 600 C

Q4

A wire has a resistance of $16\ \Omega$. A second wire, made of the same material, has half the length and half the cross-sectional area.

What is the resistance of the second wire?

A $2\ \Omega$


B $4\ \Omega$

C $16\ \Omega$

D $64\ \Omega$

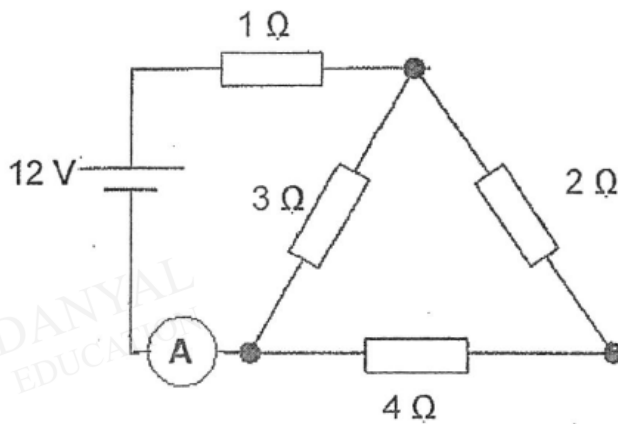Q5

The circuit diagram shows four resistors connected to a battery of 12 V, with negligible internal resistance.




What is the reading on the ammeter?

- A 1.2 A B 3.0 A C 4.0 A D 6.0 A

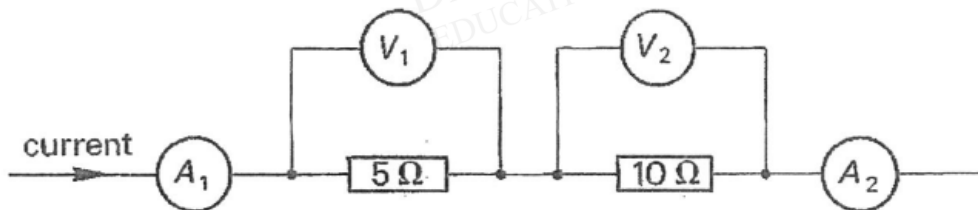Q6

Current flows in two resistors connected in series as shown in the diagram below. A_1 and A_2 are the readings on the ammeters. V_1 and V_2 are the readings on the voltmeters.



Which of the following correctly describes the ammeter and voltmeter readings?

	ammeter readings	voltmeter readings
A	A_1 is equal to A_2	V_1 is equal to V_2
B	A_1 is equal to A_2	V_1 is less than V_2
C	A_1 is greater than A_2	V_1 is equal to V_2
D	A_1 is less than A_2	V_1 is less than V_2

Answers

Current and DC Circuits Test 2.0

Q1 D

Q2 C

Q3 D

Q4 C

Q5 D

Q6 B

Q7 B

Q8 C

Q9 A

Q10 C

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION