

O Level Combined Physics Structured

Current and DC Circuits Test 3.0

Q1

Fig. 8.1 shows a circuit in which all the switches are opened.

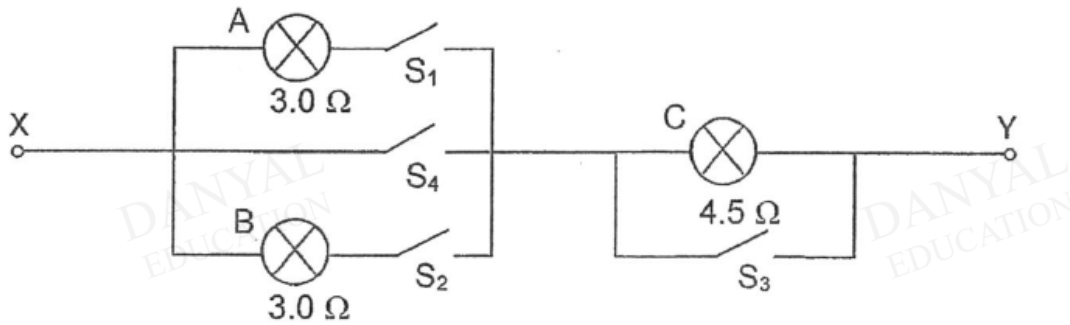


Fig. 8.1

- (a) Calculate the effective resistance between X and Y when S₁ and S₂ are closed.

effective resistance = _____ Ω [2]

- (b) Suggest which light bulb(s) will light up when all switches are closed. Explain your answer.


[2]

DANYAL
EDUCATION

DANYAL
EDUCATION

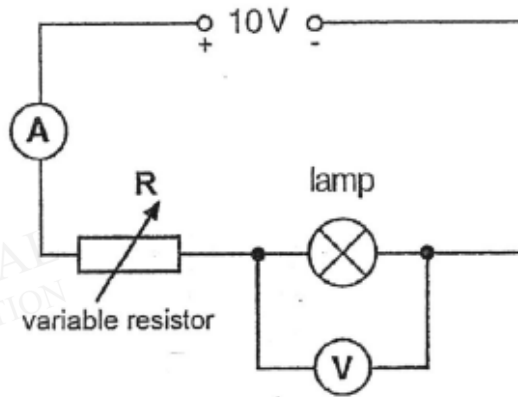Q2

The battery in the circuit below has an e.m.f. of 10 V and negligible resistance. The variable resistor **R** is adjusted until the voltmeter reading is 2.5 V and the ammeter reading is 0.5 A.



(a) Determine the resistance of the light bulb.

resistance = [2]

(b) Calculate the resistance of the variable resistor **R**.

resistance = [2]

(c) The resistance of the variable resistor **R** is now increased to 45 Ω .

Assuming that the resistance of the light bulb in (a) remains unchanged, state and explain what happens to the brightness of the light bulb.

.....
.....
..... [2]

Q3

Three resistors are arranged in parallel as shown in the circuit in Fig. 10.1.

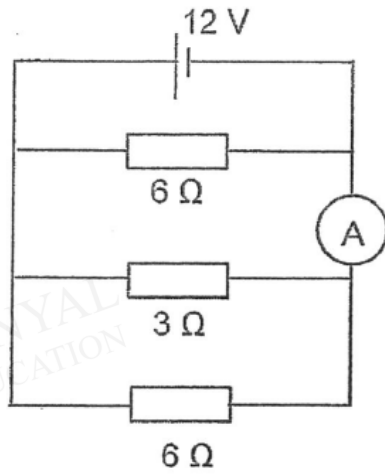


Fig 10.1

a) What is the total resistance of the circuit?

total resistance = Ω [2]

b) What is the total circuit current?

total current = A [2]

c) What is the reading in the ammeter?

ammeter reading = A [1]

Q4

The circuit in Fig. 8 was completed with 1 e.m.f. source, E and 3 resistors placed as shown. Potential difference across X and Y is 18 V.

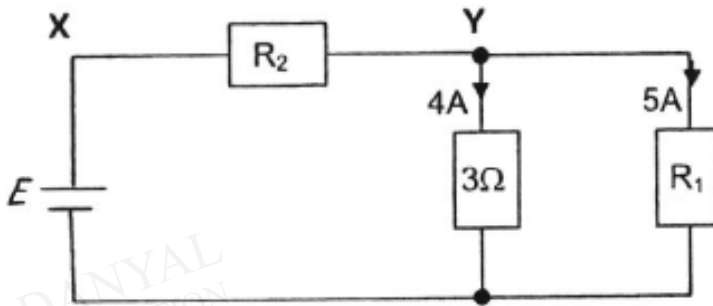


Fig. 8

(a) What is the resistance, R_1 ? [2]

(b) What is the resistance R_2 ? [2]

(c) What is the e.m.f., E ? [2]

Q5

Fig. 7.1 shows an electrical circuit containing four resistors R_1 , R_2 , R_3 and R_4 connected to a 12 V cell.

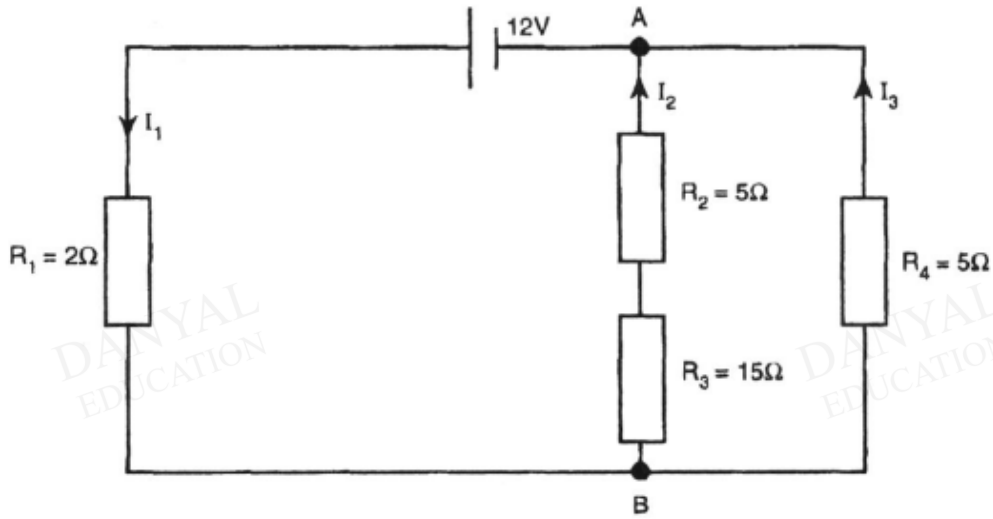


Fig. 7.1

Calculate

(a) the effective resistance of the circuit,

effective resistance = [2]

(b) the potential difference across R_1 , R_2 and R_4 ,

p.d. across R_1 =

p.d. across R_2 =

p.d. across R_4 = [3]

Answers

Current and DC Circuits Test 2.0

Q1

(a) Effective resistance = $(1/3 + 1/3)^{-1} + 4.5$ = 6.0 Ω	[1] [1]
(b) When all switches are closed, <u>the light bulbs will not light up</u> as there is a <u>short circuit</u> .	[1] [1]

Q2

(a) $R = V/I$ = 2.5/0.5 = 5 Ω	1 1
(b) P.d. across variable resistor = 7.5 V $R = V/I$ = 7.5/0.5 = 15 Ω	1 1
(c) The potential difference of the lamp will decrease / current decrease This leads to a decrease in the brightness of the lamp.	1 1

Q3

1a	Total R = $(1/3 + 1/6 + 1/6)^{-1}$ = 1.5 Ω	M1 A1
1b	Total current = V / R = 12/1.5 = 8 A Can also use ohm's law to find individual branch current and sum up.	M1 A1
1c	Reading = 4 A + 2 A = 6 A	A1

Q4

The circuit in Fig. 8 was completed with 1 e.m.f. source, E and 3 resistors placed as shown. Potential difference across X and Y is 18 V.

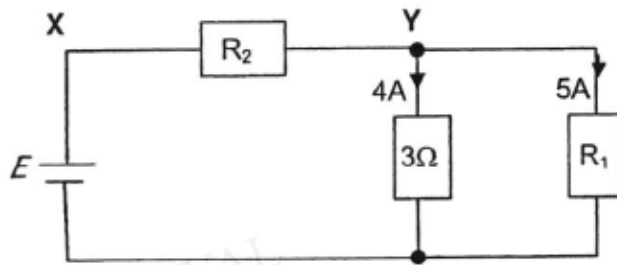


Fig. 8

- (a) What is the resistance, R_1 ?

[2]

$$\text{Pd across } 3\Omega = \text{pd across } R_1 \quad [1]$$

$$4 \times 3 = 5 \times R_1$$

$$R_1 = 12 / 5 = 2.4 \Omega \quad [1]$$

- (b) What is the resistance R_2 ?

[2]

$$\text{Total current flowing through } R_2 = 9 \text{ A}$$

$$R_2 = 18 / 9 = 2 \Omega \quad [1]$$

- (c) What is the e.m.f., E ?

[2]

$$\text{Emf} = \text{pd across } XY + \text{pd across } 3\Omega$$

$$= 18 \text{ V} + 3(4) \quad [1]$$

$$= 30 \text{ V} \quad [1]$$

Q5

(a) the effective resistance of the circuit,

$$\frac{1}{R_s} = \frac{1}{20} + \frac{1}{5}$$

$$= \frac{5}{20}$$

$$R_s = 4 \Omega \quad [1]$$

$$R_T = 2 + 4 = 6 \Omega \quad [1]$$

effective resistance = [2]

(b) the potential difference across R_1 , R_2 and R_4 ,

$$I_1 = \frac{V_T}{R_T}$$

$$= \frac{12}{6}$$

$$= 2.0 \text{ A} \quad [1]$$

Hence p.d. across $R_1 = 2 \text{ A} \times 2 \Omega = 4 \text{ V} \quad [1]$

$I_2 = 5/25 \times I_1 = 0.4 \text{ A}$, hence p.d. across $R_2 = 0.4 \text{ A} \times 5 \Omega = 2 \text{ V} \quad [1]$

$I_3 = 20/25 \times I_1 = 1.6 \text{ A}$, hence p.d. across $R_4 = 1.6 \text{ A} \times 5 \Omega = 8 \text{ V} \quad [1]$