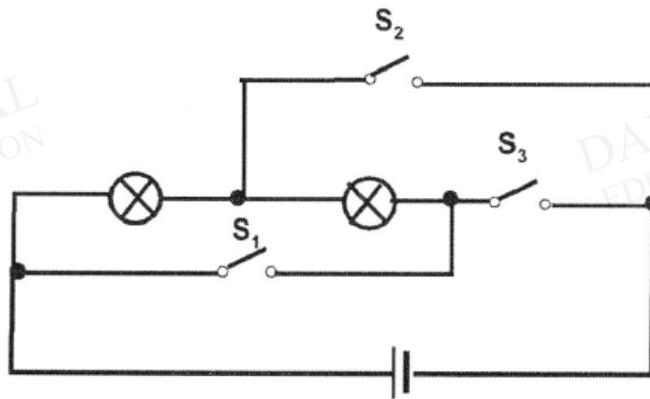


O Level Pure Physics MCQs

Current and DC Circuits Test 2.0

Q1

Two identical light bulbs and three switches S_1 , S_2 , and S_3 are connected together to a battery in the circuit shown below.



To connect the two bulbs together in parallel, which switch/es should be closed?

- A S_1
- B S_1, S_2
- C S_2
- D S_2, S_3


Q2

A piece of wire **X** that is made of a certain material has a resistance of 16Ω . What is the resistance of another piece of wire **Y** of the same material with half the diameter and twice the length of wire **X**?





- A 2.0Ω
- B 12Ω
- C 32Ω
- D 128Ω

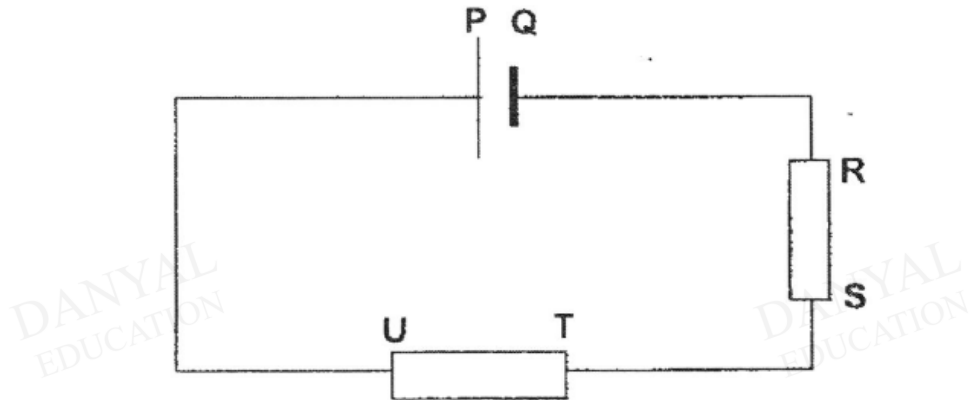Q3

The diagram shows two resistors connected in series to a cell with wires of negligible resistance. The ends of the cell and resistors are marked P, Q, R, S, T and U correspondingly.




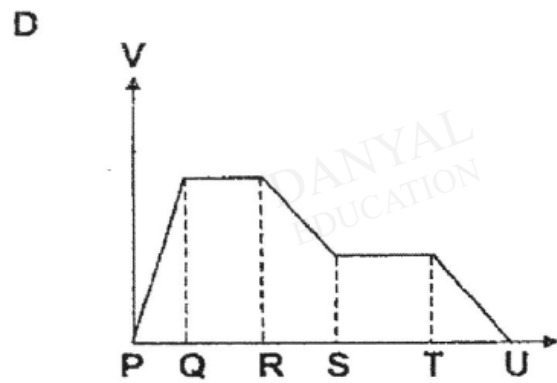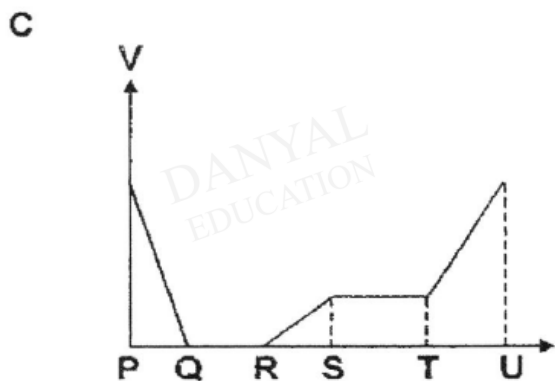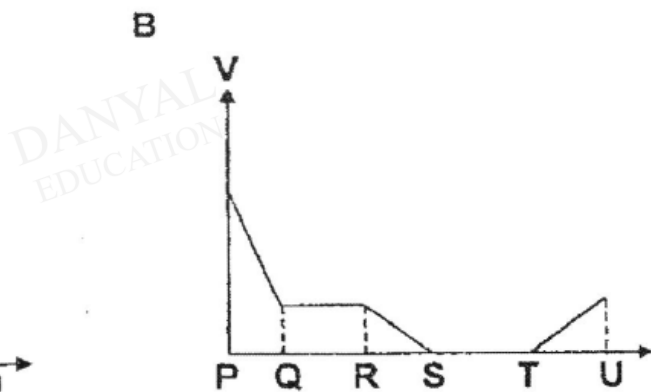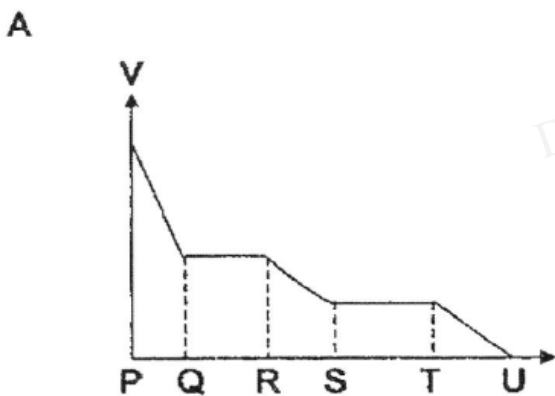Which of the following graphs correctly shows how the potential, V , vary in the regions PQRSTU?



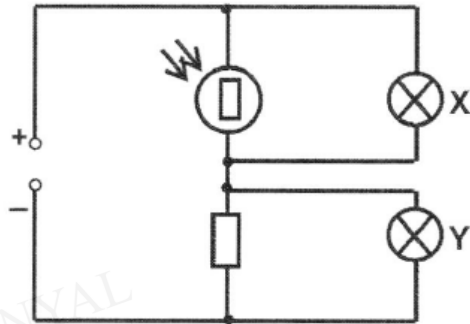Q4

The diagram below shows an electrical circuit consisting of an LDR, a fixed resistor and two identical light bulbs connected to a power supply.




What will happen to the brightness of bulb X and Y when the light incident on the LDR decreases?

	<u>Bulb X</u>	<u>Bulb Y</u>
A	brighter	dimmer
B	brighter	brighter
C	dimmer	brighter
D	dimmer	same

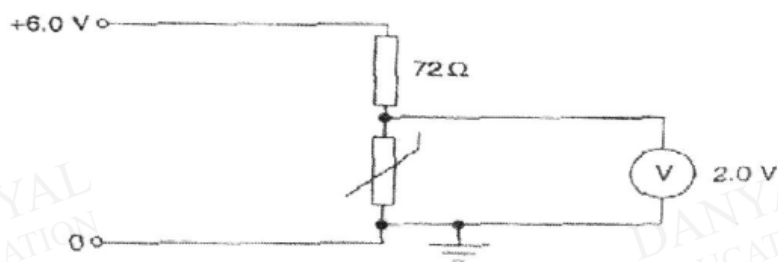Q5

A thermistor is connected in series with a $72\ \Omega$ resistor across a constant $6.0\ \text{V}$ power supply. When the temperature of the thermistor is $30\ ^\circ\text{C}$, the potential difference across it is $2.0\ \text{V}$.



What is the resistance of the thermistor at $30\ ^\circ\text{C}$?

- | | | | |
|---|---------------|---|---------------|
| A | $28\ \Omega$ | B | $36\ \Omega$ |
| C | $108\ \Omega$ | D | $148\ \Omega$ |

Q6

Two identical lamp each is labelled 230 V, 100 W are connected to a 230 V mains supply in series.

What is the current flowing through each lamp?

- | | | | |
|----------|--------|----------|--------|
| A | 0.22 A | B | 0.43 A |
| C | 0.87 A | D | 2.3 A |


Q7

Why is tungsten preferred to copper when choosing the material for the filament of an electric light bulb?

- A** Tungsten has a lower resistance than copper
- B** Tungsten is less likely to combust
- C** Tungsten has a higher melting point than copper
- D** Tungsten is more malleable than copper

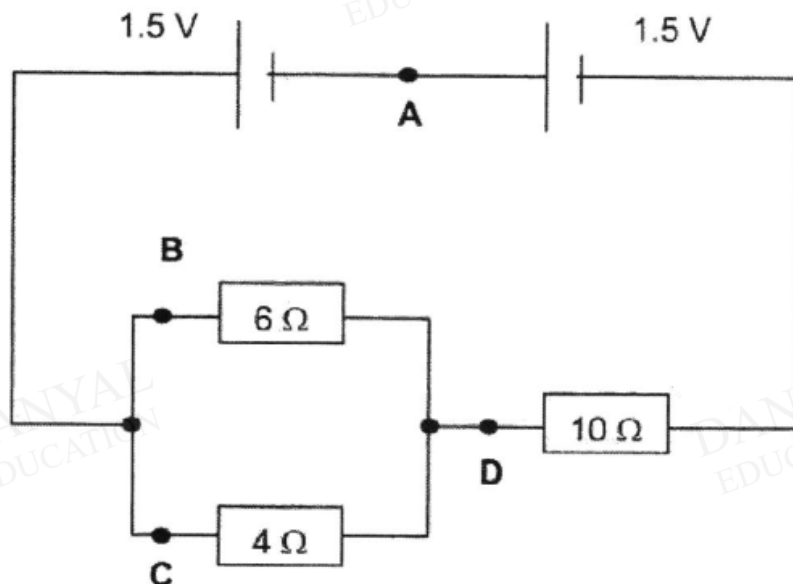Q8

In the circuit shown, at which point, A, B, C or D, is the current the smallest?



Q9

One of the following electrical appliances has the largest working resistance. Which one is it?

	Electrical appliance	Power (W)	Voltage(V)
A	Washing machine	3000	250
B	Electric fan	750	240
C	Electric iron	120	240
D	Car headlamp	50	12

Q10

The resistance of a wire is 1.00Ω at ice point and 1.40Ω at steam point.

What is the resistance of the wire at 200°C ?

- A** 1.80Ω
- B** 1.96Ω
- C** 2.00Ω
- D** 2.80Ω

Answers

Current and DC Circuits Test 2.0

- Q1 B
- Q2 D
- Q3 C
- Q4 A
- Q5 B
- Q6 A
- Q7 C
- Q8 B
- Q9 C
- Q10 A

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION