

O Level Pure Physics MCQs

Current and DC Circuits Test 5.0

Q1


3 J of energy is dissipated from a circuit when 6 C of charge flows through the cell.

What is the e.m.f. of the cell?

- A 0.5 V B 2 V C 4 V D 18 V

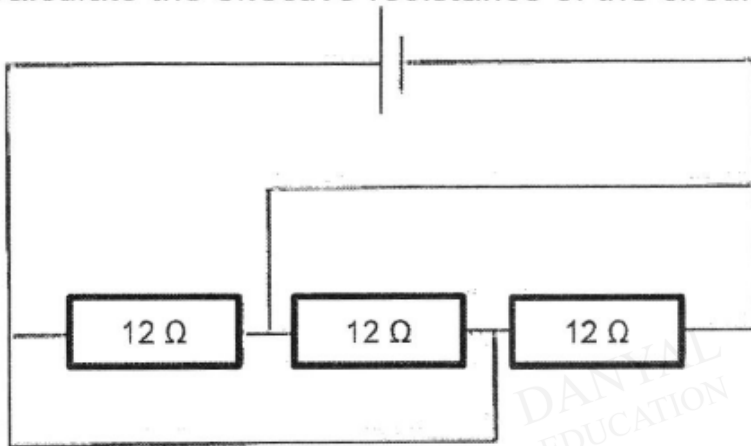Q2


Calculate the effective resistance of the circuit.



- A 4 Ω B 12 Ω C 18 Ω D 36 Ω

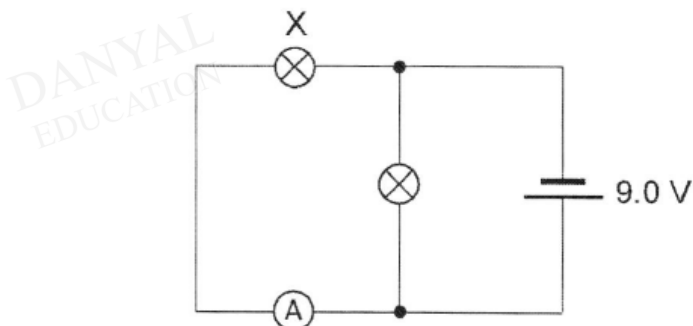Q3

The diagram below shows a circuit which consists of a cell, an ammeter and two bulbs. The ammeter reading is 2.0 A and both bulbs are **not** identical.



What is the potential difference across the bulb X?

- A 2.0 V B 4.5 V C 9.0 V D 18 V

Q4
Diagram 1 shows a potential divider circuit containing two $100\ \Omega$ resistors.

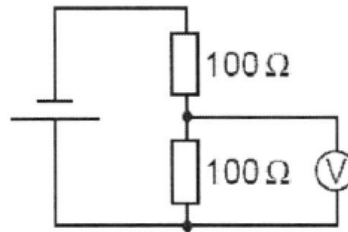


Diagram 1

One of the resistors is changed to $90\ \Omega$, as shown in diagram 2.

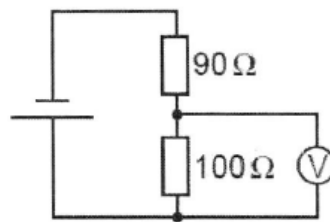


Diagram 2

How does the reading in the voltmeter change when this is done?

- A It becomes zero.
- B It decreases a little.
- C It increases a little.
- D It stays the same.

Q5
A series circuit consists of two cells and two fixed resistors. The current in the circuit needs to be increased. Which of the following actions **cannot** do so?


- A replace the existing wires with thicker wires
- B shorten the existing wires
- C remove one of the resistors
- D connect the two cells in parallel to each other in the circuit

Q6
Which of the following is equivalent to one coulomb?

- A one ampere per volt
- B one ampere second
- C one volt ampere
- D one volt per ampere

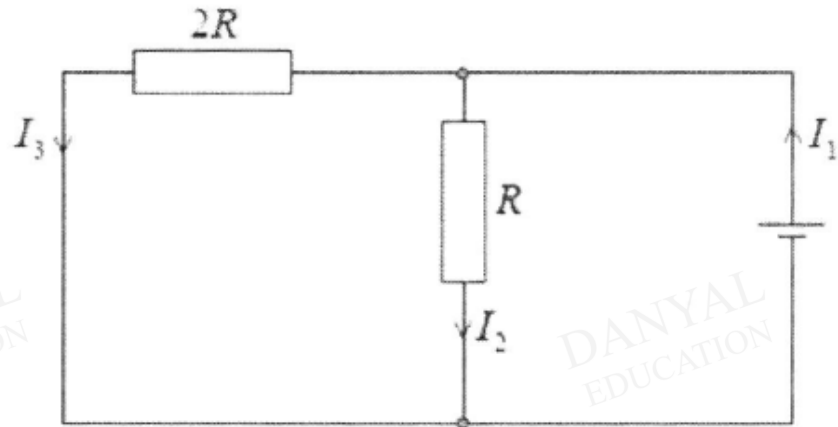Q7

In the circuit shown below, the cell has negligible internal resistance.




Which of the following equations is correct?


- A $I_1 = 2I_2$
- B $I_1 = 2I_3$
- C $I_2 = 2I_3$
- D $I_3 = 2I_1$

Q8


In the circuits below, the cells each have the same e.m.f. and zero internal resistance. All the resistors have the same resistance.

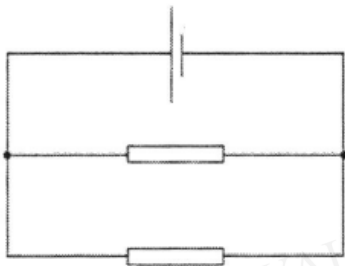

circuit X

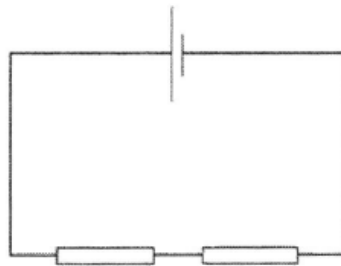

circuit Y

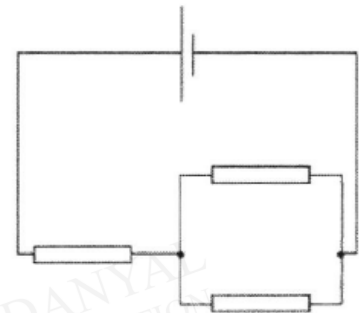

circuit Z


Which of the following gives the current through the cells in order of increasing magnitude?

	lowest current	→	highest current
A	X	Y	Z
B	Z	X	Y
C	Y	Z	X
D	Y	X	Z

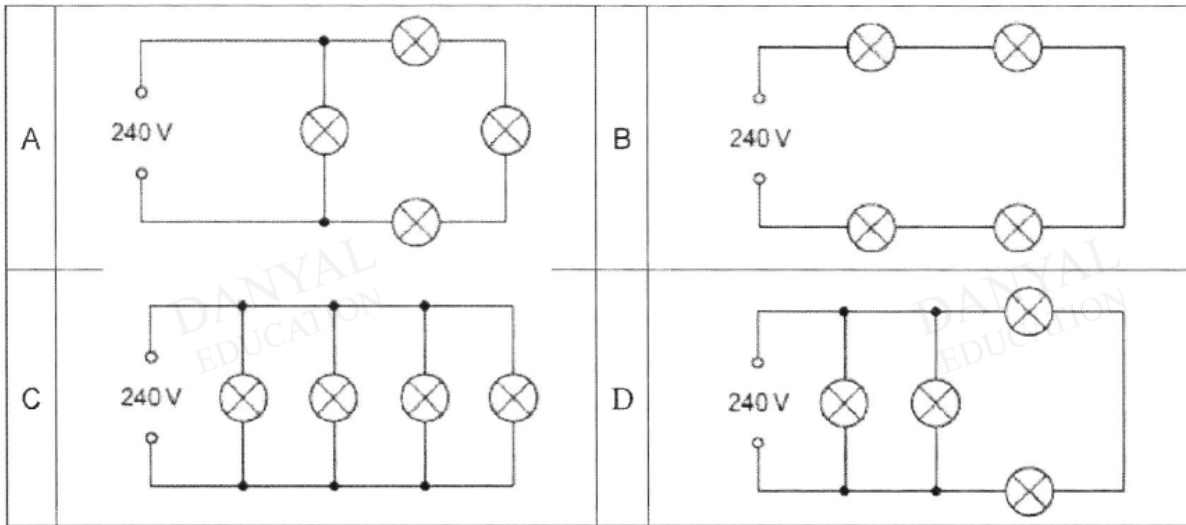Q9


Four lamps are each labelled 240 V.

In which circuit do all four lamps have normal brightness?



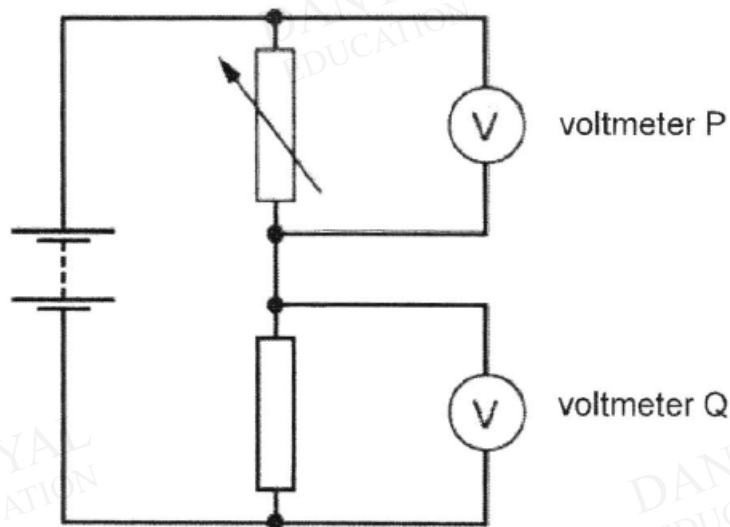Q10

The diagram shows a potential divider connected to two voltmeters P and Q.



The resistance of the variable resistor is decreased.

Which option shows what happens to the reading on each voltmeter?

	reading on Voltmeter P	reading on Voltmeter Q
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases

Answers

Current and DC Circuits Test 5.0

Q1 A

Q2 A

Q3 C

Q4 C

Q5 D

Q6 B

Q7 C

Q8 C

Q9 C

10 B

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION

DANYAL
EDUCATION